

ELEC 342 Lab 1

AC/DC Circuits and Basic Measurements

Manav Khangura

Warrick Lo

Yuvraj Chadha

09 February 2026

Contents

Pre-Lab	2
Lab	5
Task 1	5
Task 2	6
Task 3	9
Task 4	10
Appendix	11
Code Listings	11
Images	13

List of Tables

1	Single-phase parallel inductors	5
2	Single-phase parallel capacitors	5
3	Parallel connection of RLC components	5
4	Series connection of RLC components	6
5	Balanced and unbalanced wye-connected RL three-phase load	7
6	Balanced and unbalanced delta-connected RL three-phase load	8
7	Two-wattmeter measurements with delta-connected RL three-phase load	9
8	Single-phase full-wave rectifier, without a capacitor filter	9
9	Single-phase full-wave rectifier, with a capacitor filter	9
10	Three-phase full-wave rectifier, without a capacitor filter	10
11	Three-phase full-wave rectifier, with a capacitor filter	10

List of Figures

1	Phasor view of circuit with three resistors, one inductor, and three capacitors	7
2	Phasor measurements for the RL load box with three inductors	13
3	Phasor measurements for the RC load box with three capacitors	13
4	Measurements of parallel connections of RLC components	14
5	Measurements of series connections of RLC components	14
6	Three-phase measurements with wye-connected RL load box	15
7	Three-phase measurements with delta-connected RL load box	17
8	Two-wattmeter measurements with delta-connected RL load box	18
9	Single-phase full-wave rectifier, without and with capacitor filter	19
10	Three-phase full-wave rectifier, without and with capacitor filter	20

Pre-Lab

Warrick Lo, 09 February 2026

Using $S = P + jQ = VI$, we get

$$S = I^2 Z = I^2 (R + jX) \quad \text{and}$$

$$S = \frac{V^2}{Z} = \frac{V^2}{R + jX}.$$

Thus, we can solve for P and Q when the impedances are all either purely resistive or reactive:

$$P = I^2 R, \quad (1a)$$

$$= \frac{V^2}{R}, \quad \text{and} \quad (1b)$$

$$Q = I^2 X, \quad (1c)$$

$$= \frac{V^2}{X}. \quad (1d)$$

Using the power triangle and the definition of the power factor angle,

$$\cos \varphi = \frac{P}{S}, \quad \tan \varphi = \frac{Q}{P},$$

and thus,

$$Q = P \tan \varphi. \quad (2)$$

Resistance

Series resistance:

$$R = \frac{P}{I^2} \quad \text{Using equations (1a) and (2)} \quad (3a)$$

Parallel resistance:

$$R = \frac{V^2}{P} \quad \text{Using equations (1b) and (2)} \quad (3b)$$

Inductance

$$jX_L = j\omega L$$

$$L = \frac{X_L}{\omega} \quad (4)$$

Series inductance:

$$\begin{aligned} L &= \frac{Q}{\omega I^2} && \text{Using equations (1c) and (4)} \\ &= \frac{P \tan \varphi}{\omega I^2} && \text{Using equation (2)} \\ &= \frac{P \tan \varphi}{2\pi f I^2} && (5a) \end{aligned}$$

Parallel inductance:

$$\begin{aligned}
 L &= \frac{V^2}{\omega Q} && \text{Using equations (1d) and (4)} \\
 &= \frac{V^2}{\omega P \tan \varphi} && \text{Using equation (2)} \\
 &= \frac{V^2}{2\pi f P \tan \varphi} && (5b)
 \end{aligned}$$

Capacitance

$$\begin{aligned}
 -jX_C &= \frac{1}{j\omega C} = \frac{-j}{\omega C} \\
 C &= \frac{1}{\omega X_C} && (6)
 \end{aligned}$$

Series capacitance:

$$\begin{aligned}
 C &= \frac{I^2}{\omega Q} && \text{Using equations (1c) and (6)} \\
 &= \frac{I^2}{\omega P \tan \varphi} && \text{Using equation (2)} \\
 &= \frac{I^2}{2\pi f P \tan \varphi} && (7a)
 \end{aligned}$$

Parallel capacitance:

$$\begin{aligned}
 L &= \frac{Q}{\omega V^2} && \text{Using equations (1d) and (6)} \\
 &= \frac{P \tan \varphi}{\omega V^2} && \text{Using equation (2)} \\
 &= \frac{P \tan \varphi}{2\pi f V^2} && (7b)
 \end{aligned}$$

Instantaneous Power

$$\cos \alpha \cos \beta = \frac{1}{2} (\cos(\alpha + \beta) + \cos(\alpha - \beta)) \quad (8)$$

$$\begin{aligned}
 v(t) &= \sqrt{2} V_{\text{RMS}} \cos(\omega t + \varphi_v) \\
 i(t) &= \sqrt{2} I_{\text{RMS}} \cos(\omega t + \varphi_i)
 \end{aligned}$$

$$\begin{aligned}
 p(t) &= v(t)i(t) \\
 &= 2V_{\text{RMS}}I_{\text{RMS}} \cos(\omega t) \cos(\omega t + \varphi) \\
 &= V_{\text{RMS}}I_{\text{RMS}} (\cos \varphi + \cos(2\omega t + \varphi)) && (9)
 \end{aligned}$$

Complex Power

$$\begin{aligned}
 S &= P + jQ \\
 &= VI \cos \varphi + jVI \sin \varphi \\
 P &= VI \cos \varphi && (10a)
 \end{aligned}$$

$$Q = VI \sin \varphi \quad (10b)$$

Three-Phase Power

$$V_{\text{line}} = \sqrt{3}V_{\text{phase}}$$

$$P = 3V_{\text{phase}}I_{\text{phase}} \cos \varphi \quad (11a)$$

$$= \sqrt{3}V_{\text{line}}I_{\text{line}} \cos \varphi \quad (11b)$$

$$Q = 3V_{\text{phase}}I_{\text{phase}} \sin \varphi \quad (12a)$$

$$= \sqrt{3}V_{\text{line}}I_{\text{line}} \sin \varphi \quad (12b)$$

Task 1A. Measurements with RL Load Box

Measurement	$V_{I(RMS)}$ (V)	$I_{I(RMS)}$ (A)	φ_1 (°)	$P_{I(AVG)}$ (W)	Z_{eq} (Ω)	$R_{eq(series)}$ (Ω)	L_{eq} (mH)
One inductor	14.11	0.64	85.4	0.72	22.18	1.758	57.95
Three inductors	14.07	1.98	85.2	2.33	7.11	0.594	18.77

Table 1. Single-phase parallel inductors.

- **How is this inductor different from an ideal inductor element?**

The inductor has many parasitic elements, including physical resistance from the metal conductor, self-capacitance, magnetic flux leakage, radiation losses at high frequencies, and core losses if it's not an air-core inductor.

- **Are the calculated values of inductance close to the expected value? What is the difference?**

The nominal value for each inductor, as indicated on the load box, is 40 mH. With three inductors in parallel, this gives us an equivalent inductance of 13.33 mH. The measured values are higher, at 57.95 mH for the single inductor and 18.77 mH for the parallel inductors, giving a deviation of 45 % and 41 %, respectively. This is a relatively high amount of deviation and can be attributed to the parasitic properties of the inductor described above.

Task 1B. Measurements with RC Load Box

Measurement	$V_{I(RMS)}$ (V)	$I_{I(RMS)}$ (A)	φ_1 (°)	$P_{I(AVG)}$ (W)	Z_{eq} (Ω)	$R_{eq(parallel)}$ (Ω)	C_{eq} (μ F)
One capacitor	14.07	0.22	-89.6	0.022	62.82	0.4545	40.74
Three capacitors	14.12	0.68	-89.8	0.034	20.47	0.0735	125.9

Table 2. Single-phase parallel capacitors.

- **How is this capacitor different from an ideal capacitor element?**

The capacitor has physical resistance from the metal conductor, self-inductance, fringing field losses, leakage current through the dielectric, and the skin effect at high frequencies, among other losses.

- **Are the calculated values of capacitance close to the expected value? What is the difference?**

The nominal value for each capacitor, as indicated on the load box, is 40 μ F. With three capacitors in parallel, the equivalence capacitance is 120 μ F. The measured values are slightly higher, at 40.74 μ F for the single capacitor and 125.9 μ F for the parallel capacitors. This gives us a deviation of 1.9 % and 4.9 %, respectively, which is a reasonably low amount of deviation that can be attributed to the real-world properties of the capacitor described earlier.

Task 1C. Parallel Connection of RLC Components

Measurement	$I_{1(RMS)}$ (A)	φ_1 (°)	$I_{2(RMS)}$ (A)	φ_2 (°)	$I_{3(RMS)}$ (A)	φ_3 (°)	$P_{I(AVG)}$ (W)
R_1	0.71	0.2	—	—	—	—	10.0
R_1 and L_1	0.99	39.8	0.64	85.2	—	—	10.7
R_1, L_1, C_1, C_2, C_3	0.79	-1.0	0.63	85.1	0.67	-89.5	10.7

Table 3. Parallel connection of RLC components. Supply voltage $V_1 = 14.16 \angle -1.7^\circ$ V RMS.

- **How has the real power changed when you connected inductors and capacitors in parallel?**

In the ideal scenario, adding inductors and capacitors to the circuit wouldn't change the real power as the components are purely reactive. However due to the parasitic resistances of the components, they consume small amounts of real power. The total real power of the circuit is then simply the sum of the resistor's real power and the reactive components' real power from losses.

- **How are the magnitudes of the currents I_1 , I_2 , and I_3 related to each other when all elements are connected in parallel?**

The current I_1 is the sum of all three branch currents as phasors:

$$\tilde{I}_1 = \tilde{I}_R + \tilde{I}_L + \tilde{I}_C.$$

In the ideal model, the inductor and capacitor currents are, respectively, 90° and -90° out of phase from the resistor current. Since they are 180° apart, the magnitudes will subtract from each other. Thus the magnitude of the current I_1 can be given by

$$|\tilde{I}_1| = \sqrt{|\tilde{I}_R|^2 + (|\tilde{I}_2| - |\tilde{I}_3|)^2}. \quad (13)$$

- **Can either I_2 and/or I_3 have a magnitude larger than the magnitude of I_1 ? Explain.**

Yes, if the resistor current is small enough, or equally if both inductor and capacitor currents are large enough. We can see this in equation (13); the reactive components' currents "nearly cancel" each other out, giving only a small increase to I_1 , but they can each be larger than I_1 individually.

Task 1D. Series Connection of RLC Components

Measurement	$I_{1(\text{RMS})}$ (A)	φ_1 ($^\circ$)	$V_{2(\text{RMS})}$ (V)	φ_2 ($^\circ$)	$V_{3(\text{RMS})}$ (V)	φ_3 ($^\circ$)	$P_{1(\text{AVG})}$ (W)
R_1, L_1, C_1	0.32	55.3	8.65	218.3	20.58	31.2	2.3
R_1, L_1, C_1, C_2, C_3	0.64	0.8	14.25	80.6	13.97	90.5	9.0
$R_1, R_2, R_3, L_1, C_1, C_2, C_3$	1.56	25.3	27.17	245.0	34.08	60.6	19.5

Table 4. Series connection of RLC components. Supply voltage $V_1 = 14.14\angle -1.6^\circ$ V RMS.

- **How has the real power changed when you connected capacitors in parallel or resistors in parallel?**

When the capacitors are connected in parallel, the equivalent impedance of the capacitors is significantly lowered. This matches with how we see V_3 being lower afterwards. Thus, more current is flowing through the circuit and more power is being dissipated by the resistor. When the resistors are connected in parallel, more current is again going through the circuit and thus the real power increases as well.

- **How are the magnitudes of voltages V_1 , V_2 , and V_3 related to each other when all elements are connected in series?**

The voltage V_1 is the sum of all three components' voltages as phasors:

$$\tilde{V}_1 = \tilde{V}_R + \tilde{V}_L + \tilde{V}_C.$$

In the ideal model, the inductor and capacitor voltages are, respectively, 90° and -90° out of phase from the resistor voltage. Since they are 180° apart, the magnitudes will subtract from each other. Thus the magnitude of the voltage V_1 can be given by

$$|\tilde{V}_1| = \sqrt{|\tilde{V}_R|^2 + (|\tilde{V}_2| - |\tilde{V}_3|)^2}. \quad (14)$$

- **Can either V_2 and/or V_3 have a magnitude larger than the magnitude of V_1 ? Explain.**

Yes, if the resistor voltage is small enough, or equally if both inductor and capacitor voltages are large enough. Similar to Task 1C, we can see how according to equation (14), the reactive components' voltages "nearly cancel" each other out, which allows V_2 and V_3 to be each larger than V_1 individually.

- **Support your answer with the phasor diagram corresponding to the measurement Task 1D, step 5.**

See figure 1.

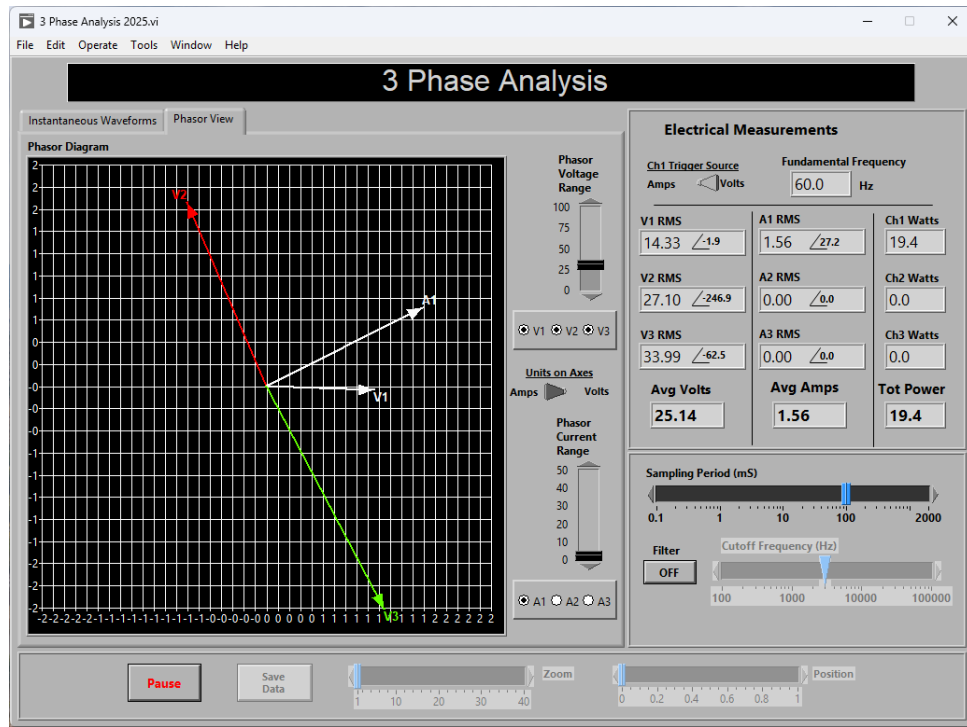


Figure 1. Phasor view of circuit with three resistors, one inductor, and three capacitors.

Task 2A. Three-Phase Measurements with Wye-Connected RL Load Box

Measurement	Phase 1 (RMS)		Phase 2 (RMS)		Phase 3 (RMS)		Total
	$V_{\Delta\phi_v}$ (V)	$I_{\Delta\phi_i}$ (A)	$V_{\Delta\phi_v}$ (V)	$I_{\Delta\phi_i}$ (A)	$V_{\Delta\phi_v}$ (V)	$I_{\Delta\phi_i}$ (A)	P_{AVG} (W)
RL balanced load, neutrals disconnected	10.17 \angle 4.5	0.27 \angle -46.3	10.15 \angle -238.0	0.29 \angle 73.3	9.79 \angle -115.2	0.29 \angle -163.6	5.6
RL unbalanced load, shorted resistor, neutrals disconnected	10.06 \angle 4.4	0.38 \angle -80.0	12.91 \angle -251.8	0.39 \angle 60.8	8.94 \angle -139.9	0.26 \angle -189.0	5.2
RL unbalanced load, shorted inductor, neutrals disconnected	8.88 \angle 0.9	0.45 \angle 0.6	9.15 \angle -199.3	0.26 \angle -247.8	13.71 \angle -98.4	0.43 \angle -145.0	9.9
RL unbalanced load, shorted resistor, neutrals connected	10.16 \angle -1.5	0.4 \angle -85.7	10.31 \angle -241.4	0.3 \angle 70.2	10.19 \angle -120.6	0.30 \angle -168.8	4.6
RL unbalanced load, shorted inductor, neutrals connected	10.09 \angle -1.8	0.51 \angle -2.0	10.27 \angle -241.5	0.30 \angle 70.3	10.19 \angle -120.8	0.30 \angle -168.9	9.6

Table 5. Balanced and unbalanced wye-connected RL three-phase load.

- How close are your measurements to the ideal case when the RL load is balanced?**

In the balanced load circuit, the voltages had phase differences that were calculated to be 120.0° and maximum voltage spread of less than ± 0.38 V. Similarly, the currents had phase differences of 120.0° and variations in magnitude of ± 0.02 A. These can be attributed to the tolerances in individual components, manufacturing variations, and parasitic impedances, among other things.

- **What happens to the phase voltages and currents when the resistor is shorted in one of the phases?**
Looking at the phase current through the shorted load, the magnitude will increase due to the lower impedance from the short. That current will also lag the voltage by around 90° , due to it being a (nearly) pure inductive load. Without the neutral line connected, the phase voltages drift from the target of 10 V and the phases deviate from their nominal 120° separation.
- **What happens to the phase voltages and currents when the inductor is shorted in one of the phases?**
Looking at the phase current through the shorted load, the magnitude will again increase due to the lower impedance from the short. That current will be roughly in phase with the voltage, due to it being purely resistive. Without the neutral line connected, the phase voltages also drift from the target of 10 V and the phases again deviate from their nominal 120° separation.
- **How does connecting or disconnecting the neutral wire affect the phase voltages and currents when the load is unbalanced?**
The neutral line allows the unbalanced current to flow back to the source. This stabilises the phase voltages even when the load is unbalanced, ensuring that the magnitudes stay around 10 V and the phase differences are around 120° .

Task 2B. Three-Phase Measurements with Delta-Connected RL Load Box

Measurement	Phase 1 (RMS)		Phase 2 (RMS)		Phase 3 (RMS)		Total
	$V_{\Delta\phi_v}$ (V)	$I_{\Delta\phi_i}$ (A)	$V_{\Delta\phi_v}$ (V)	$I_{\Delta\phi_i}$ (A)	$V_{\Delta\phi_v}$ (V)	$I_{\Delta\phi_i}$ (A)	P_{AVG} (W)
RL balanced load	9.98 \angle -1.6	0.93 \angle -47.0	10.06 \angle -241.9	0.95 \angle 72.0	9.93 \angle -121.3	0.96 \angle -167.1	19.7
RL unbalanced load, shorted resistor	10.10 \angle -1.5	0.94 \angle -81.0	10.14 \angle -241.7	1.39 \angle 55.0	10.02 \angle -121.3	0.97 \angle -167.2	14.6
RL unbalanced load, shorted inductor	9.97 \angle -1.5	1.41 \angle -26.2	10.15 \angle -242.3	0.91 \angle -248.7	10.03 \angle -120.9	0.97 \angle -166.6	28.8

Table 6. Balanced and unbalanced delta-connected RL three-phase load.

- **How close are your measurements to the ideal case when the RL load is balanced?**
In the balanced load circuit, the voltages had phase differences that were calculated to be 120.0° and maximum voltage spread of less than ± 0.13 V. Similarly, the currents had phase differences of 120° and variations in magnitude of ± 0.03 A. These can be attributed to the tolerances in individual components, manufacturing variations, and parasitic impedances, among other things.
- **How do the current and power measurements (values) compare with the previous case when the balanced load was wye-connected?** The average power increases by a factor of 3, compared to the wye-connected load. This is because the power per phase in a wye-connected load is given by $(V_{line}/\sqrt{3})^2 / Z \cdot \cos \phi$, whereas the delta-connected load's power per phase is given by $V_{line}^2 / Z \cdot \cos \phi$. Similarly, the line current will increase by a factor of 3, since in wye and delta connections the line current is given by $V_{line}/(\sqrt{3}Z)$ and $\sqrt{3}V_{line}/Z$, respectively.
- **What happens to the phase voltages and currents when the resistor is shorted in one of the phases?** The phase voltages do not change, staying approximately 120° apart and having a maximum voltage spread of 0.12 V. Looking at the phase current through the shorted load, the magnitude will increase due to the lower impedance from the short. That current will also lag the voltage by around 90° , due to it being a (nearly) pure inductive load.
- **What happens to the phase voltages and currents when the inductor is shorted in one of the phases?** The phase voltages do not change, staying approximately 120° apart and having a maximum voltage spread of 0.18 V. Looking at the phase current through the shorted load, the magnitude will again increase due to the lower impedance from the short. That current will be in phase with the voltage, due to it being a purely resistive load.

Task 2C. Two-Wattmeter Measurement Method with Delta-Connected RL Load Box

Measurement	Phase 1 (RMS)		Phase 2 (RMS)		Average Power		
	$V_{\Delta\phi_V}$ (V)	$I_{\Delta\phi_i}$ (A)	$V_{\Delta\phi_V}$ (V)	$I_{\Delta\phi_i}$ (A)	P_1 (W)	P_2 (W)	P_{total} (W)
RL balanced load	17.34 \angle -0.7	0.94 \angle -76.2	17.58 \angle 59.4	0.96 \angle 42.6	4.1	15.6	19.8
RL unbalanced load, shorted resistor	17.41 \angle -0.7	0.94 \angle -110.3	17.53 \angle 59.5	1.40 \angle 25.7	-5.5	19.7	14.2
RL unbalanced load, shorted inductor	17.37 \angle -0.6	1.42 \angle -55.6	17.67 \angle 59.1	0.92 \angle 81.8	14.3	14.5	28.7

Table 7. Two-wattmeter measurements with delta-connected RL three-phase load.

- **The load circuit in Task 2B and Task 2C is identical in each step. Compare the measurements of currents and voltages of Task 2B and Task 2C. Explain the results.**

The voltages measured here are greater compared to Task 2B because we are measuring the line-to-line voltage, as opposed to the phase voltage like what was done previously. As the line and phase voltages are related to each other by $V_{\text{line}} = \sqrt{3}V_{\text{phase}} \angle 30^\circ$, the voltage supply is giving the same output voltage in both Task 2B and Task 2C (as $\sqrt{3} \cdot 10 \text{ V} \cong 17.32 \text{ V}$). We also see this through our measurement of the current; the magnitude remains relatively unchanged from Task 2B to Task 2C, while the current shows a -30° phase shift because of the change in our reference (the angle of V_1).

- **Compare the measurements of the real power of Task 2B and Task 2C. Explain the results.**

The total real power remains relatively the same, as expected, since no part of the physical circuit changed. We see that when the resistor is shorted (the load is purely inductive), P_1 is negative. This can be explained by the power factor angle being more than 90° , which will make the power, given by $P = V_{\text{line}} I_{\text{phase}} \cos \phi$, negative.

Task 3A. Single-Phase Full-Wave Rectifier

	$V_{1(\text{RMS})}$ (V)	$I_{1(\text{RMS})}$ (A)	$P_{1(\text{in})}$ (W)	$V_{3(\text{RMS})}$ (V)	$V_{3(\text{PP})}$ (V)	$I_{3(\text{RMS})}$ (A)	$I_{3(\text{PP})}$ (A)	$P_{3(\text{out})}$ (W)
No load	15.05 \angle -1.7	0.08 \angle 36.2	0.8	14.19 \angle -93.8		0.11 \angle -224.5		1.0
Light load	14.87 \angle -1.8	0.84 \angle -2.4	12.5	13.34 \angle -93.9		0.88 \angle -96.2		11.7
Heavy load	14.77 \angle -1.8	1.50 \angle -2.0	22.0	13.09 \angle -94.1		1.53 \angle -95.6		19.9

Table 8. Single-phase full-wave rectifier, without a capacitor filter.

	$V_{1(\text{RMS})}$ (V)	$I_{1(\text{RMS})}$ (A)	$I_{1(\text{PP})}$ (A)	$P_{1(\text{in})}$ (W)	$V_{3(\text{RMS})}$ (V)	$V_{3(\text{PP})}$ (V)	$I_{3(\text{RMS})}$ (A)	$I_{3(\text{PP})}$ (A)	$P_{3(\text{out})}$ (W)
No load	15.04 \angle -1.7	0.34 \angle -8.6		2.2	19.90 \angle -176.3		0.17 \angle 13.1		2.8
Light load	14.73 \angle -1.8	2.5 \angle -3.9		24.8	17.73 \angle -165.8		1.23 \angle 203.1		21.7
Heavy load	14.54 \angle -2.1	3.80 \angle -2.3		39.4	16.73 \angle -161.9		2.01 \angle -159.5		33.6

Table 9. Single-phase full-wave rectifier, with a capacitor filter.

Task 4A. Three-Phase Full-Wave Rectifier

	$I_{1(\text{RMS})}$ (A)	$V_{2(\text{RMS})}$ (V)	$V_{2(\text{PP})}$ (V)	$I_{2(\text{RMS})}$ (A)	$I_{2(\text{PP})}$ (A)	$P_{3(\text{out})}$ (W)
No load	0.09 \angle 33.3	12.18 \angle -62.2		0.16 \angle -148.3		1.5
Light load	0.65 \angle 33.3	11.99 \angle -50.1		0.86 \angle -36.7		9.9
Heavy load	1.10 \angle 34.2	11.86 \angle -40.6		1.43 \angle -32.2		16.2

Table 10. Three-phase full-wave rectifier, without a capacitor filter.

	$I_{1(\text{RMS})}$ (A)	$I_{1(\text{PP})}$ (A)	$I_{2(\text{RMS})}$ (A)	$I_{2(\text{PP})}$ (A)	$V_{3(\text{RMS})}$ (V)	$V_{3(\text{PP})}$ (V)	$I_{3(\text{RMS})}$ (A)	$I_{3(\text{PP})}$ (A)	$P_{3(\text{out})}$ (W)
No load	0.08 \angle 22.4		0.20 \angle -31.0		12.58 \angle -236.0		0.12 \angle -218.5		1.6
Light load	0.70 \angle 28.6		1.02 \angle -54.3		11.91 \angle -95.9		0.83 \angle 96.0		10.0
Heavy load	1.17 \angle 29.0		1.73 \angle -54.4		11.63 \angle -96.0		1.40 \angle -183.2		16.3

Table 11. Three-phase full-wave rectifier, with a capacitor filter.

Appendix A. Code Listings

```
1 function specan(filename)
2     % Spectrum analyser
3     %
4     % Analyse and plot the frequency spectrum of a waveform
5     % given by a tab-separated value (TSV) file.
6     %
7     % The following column headers for the TSV are assumed:
8     % time, v1, v2, v3, i1, i2, i3
9     %
10    % Time measurements are assumed to be in milliseconds.
11    % All voltages and currents are assumed to be given
12    % in Volts and Amperes, respectively.
13
14    data = readtable(filename, FileType="text", Delimiter="\t");
15
16    L = length(data.time);
17    % Assumes data is sampled at regular intervals.
18    T = 1e-3*(data.time(end)-data.time(1))/(L-1);
19    fs = 1/T;
20    % Frequency axis for plotting.
21    f = fs/L*(0:L-1);
22
23    Y1 = abs(fft(data.v1)/L);
24    Y2 = abs(fft(data.v2)/L);
25    Y3 = abs(fft(data.v3)/L);
26    Y4 = abs(fft(data.i1)/L);
27    Y5 = abs(fft(data.i2)/L);
28    Y6 = abs(fft(data.i3)/L);
29
30    figure(1);
31
32    subplot(2, 1, 1);
33    hold on;
34    plot(f, Y1, "r", LineWidth=2);
35    plot(f, Y2, "g", LineWidth=2);
36    plot(f, Y3, "b", LineWidth=2);
37    title("Frequency Spectrum of Voltage Measurements");
38    xlim([0 1e3]);
39    xlabel("Frequency, $f$ (Hz)", Interpreter="latex");
40    ylabel("$\left|\mathcal{F}\{V\}\right|$ (V)", Interpreter="latex");
41    legend("V_1", "V_2", "V_3");
42
43    subplot(2, 1, 2);
44    hold on;
45    plot(f, Y4, "r", LineWidth=2);
46    plot(f, Y5, "g", LineWidth=2);
47    plot(f, Y6, "b", LineWidth=2);
48    title("Frequency Spectrum of Current Measurements");
49    xlim([0 1e3]);
50    xlabel("Frequency, $f$ (Hz)", Interpreter="latex");
51    ylabel("$\left|\mathcal{F}\{I\}\right|$ (A)", Interpreter="latex");
52    legend("I_1", "I_2", "I_3");
53 end
```

Listing 1. Frequency spectrum analysis code.

```

1 function phasor(modulus, argument)
2     % Wrapper for quiver() that plots phasor diagrams.
3     %
4     % Expects the modulus and argument (in degrees)
5     % of a complex number.
6
7     r = modulus;
8     phi = argument * pi / 180;
9
10    % Automatic scaling is disabled.
11    quiver(0, 0, r*cos(phi), r*sin(phi), 0);
12
13    xlim([-r r]);
14    ylim([-r r]);
15 end

```

Listing 2. Phasor plot code.

```

1 #!/bin/sh
2
3 # Prepare all waveform data for MATLAB processing.
4 #
5 # This script will:
6 # 1.    sanitise the header before running MATLAB's readtable();
7 # 2.    convert line endings from DOS to UNIX; and
8 # 3.    rename files to have *.tsv file extensions.
9 #
10 # This script assumes all waveform data is tab-delimited and
11 # stored in *.txt files.
12 #
13 # Usage: ./prep.sh
14
15 files=$(ls -- *.txt)
16
17 for i in $files; do
18     printf "Converting %s\n" "$i"
19
20     # Replace the header and convert DOS line endings (CRLF)
21     # to UNIX line endings (LF).
22     sed -i -e "1c time\tv1\tv2\tv3\ti1\ti2\ti3" -e "s/\r/" "$i"
23
24     # Rename files to have TSV extensions.
25     mv "$i" "${i%.*}.tsv"
26 done

```

Listing 3. Shell script for preparing data.

Appendix B. Images

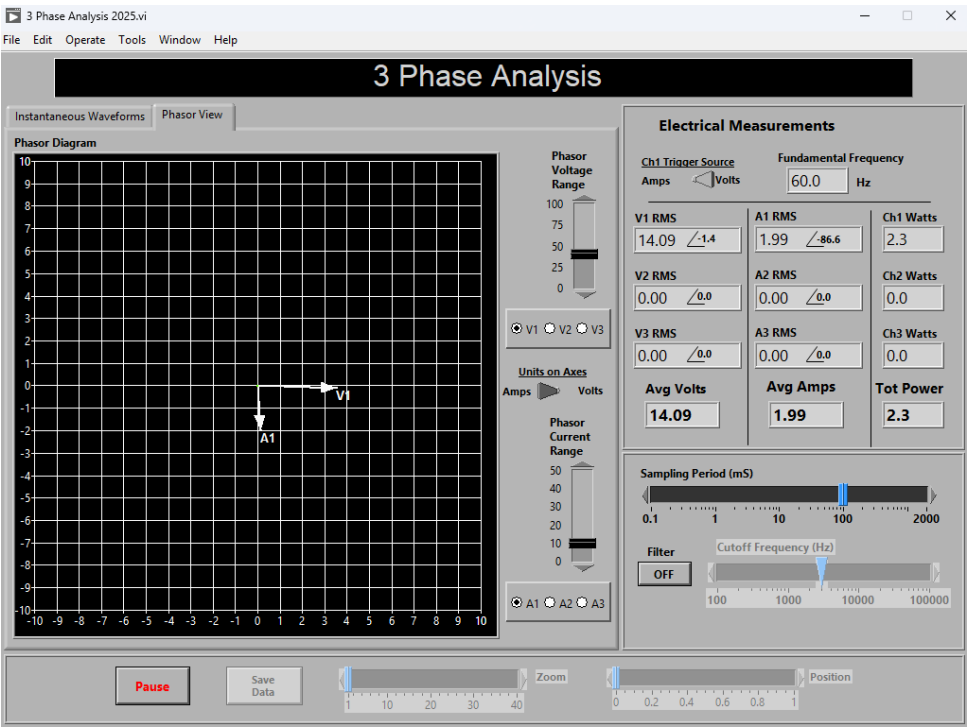


Figure 2. Phasor measurements for the RL load box with three inductors (Task 1A).

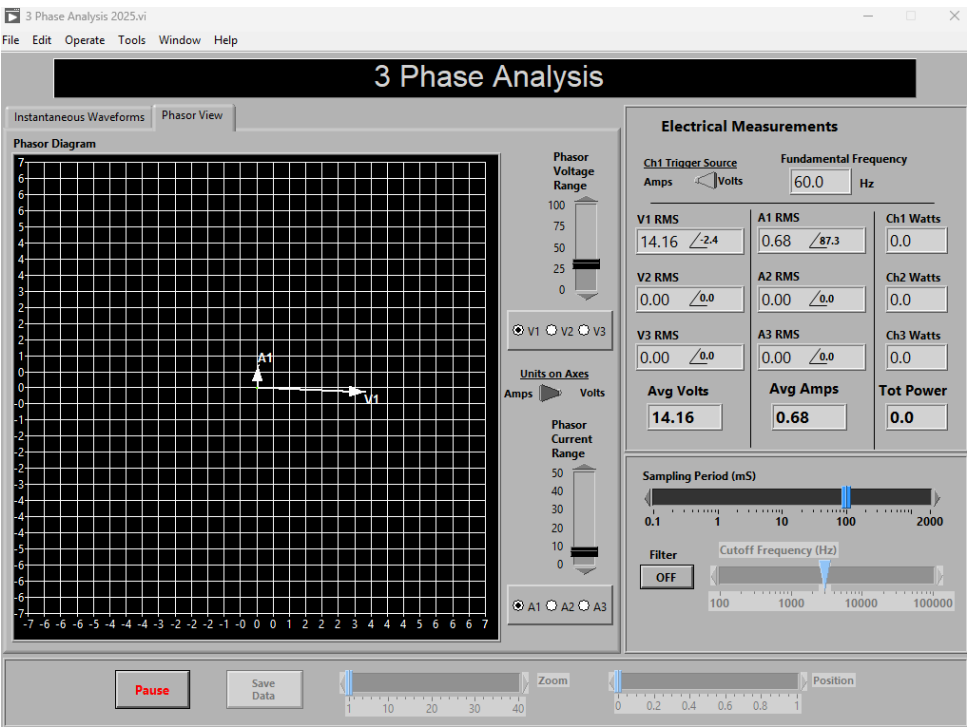


Figure 3. Phasor measurements for the RC load box with three capacitors (Task 1B).

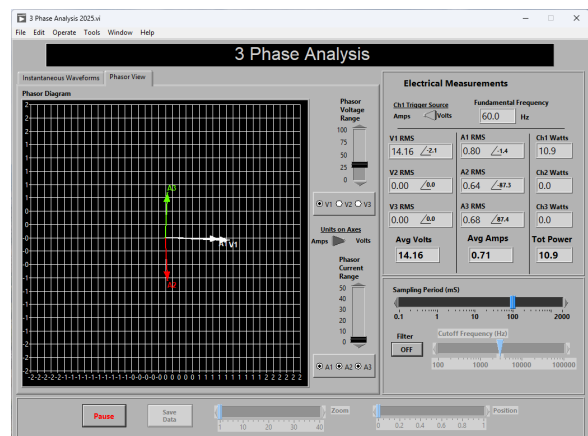
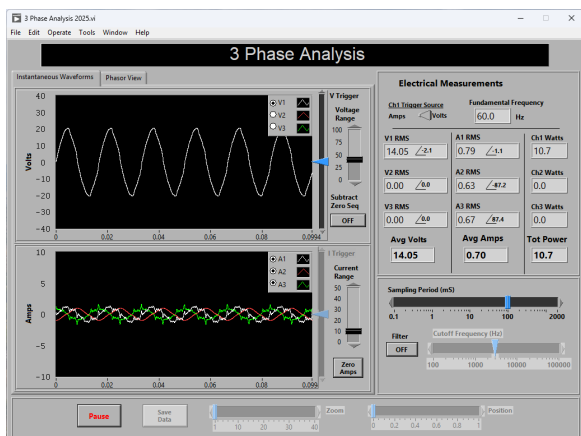
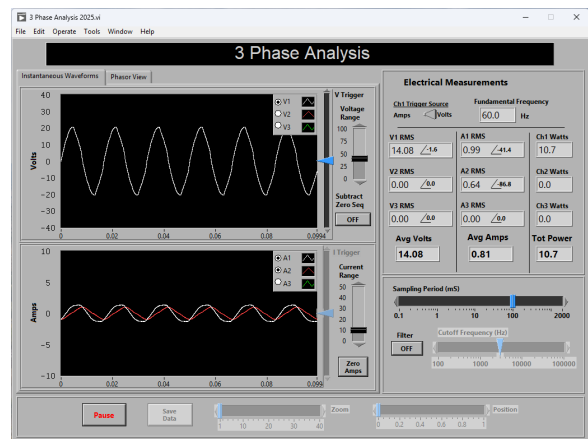
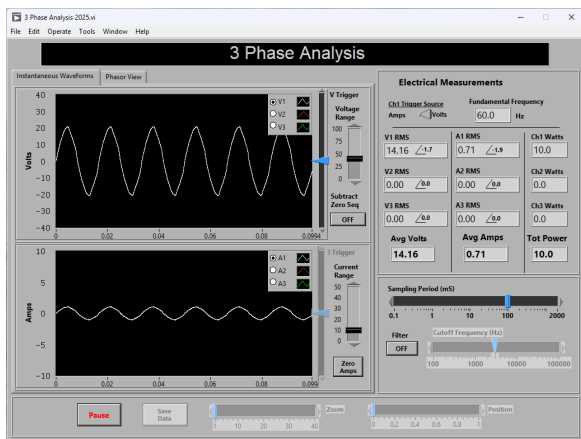


Figure 4. Measurements of parallel connections of RLC components (Task 1C).



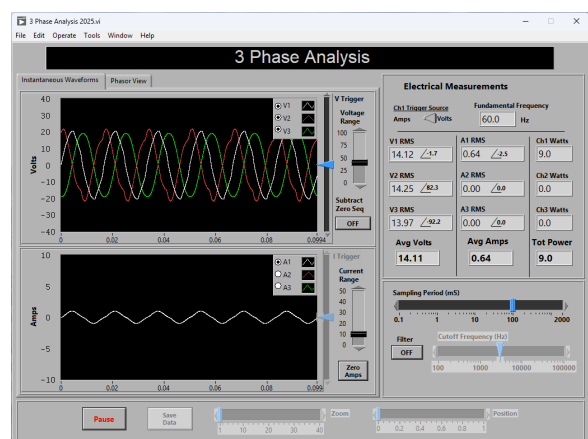
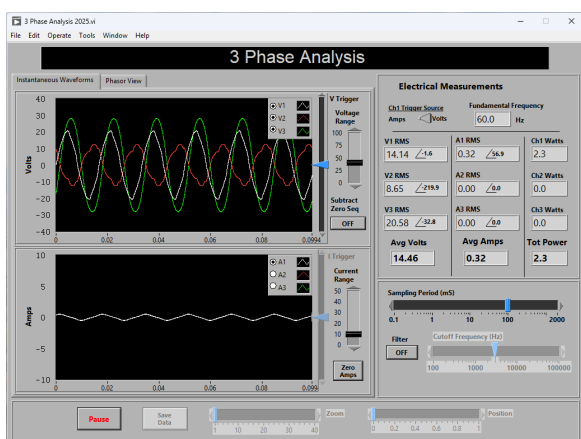


Figure 5. Measurements of series connections of RLC components (Task 1D).

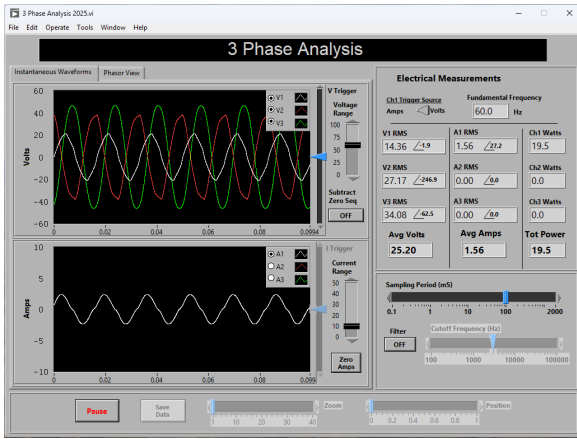


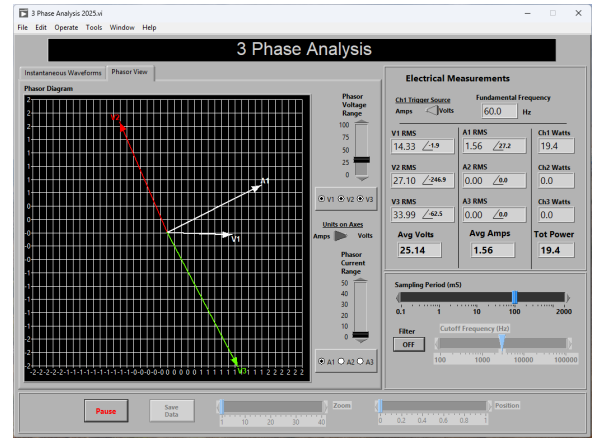(c) Waveform of circuit with three resistors, one inductor, and three capacitors.




(d) Phasor view of circuit with three resistors, one inductor, and three capacitors.


Figure 5. Measurements of series connections of RLC components (Task 1D).

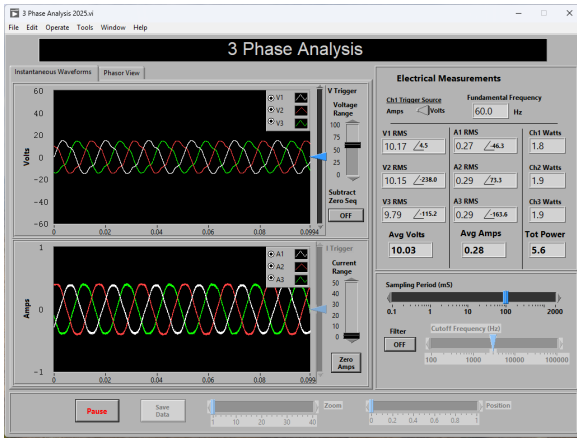

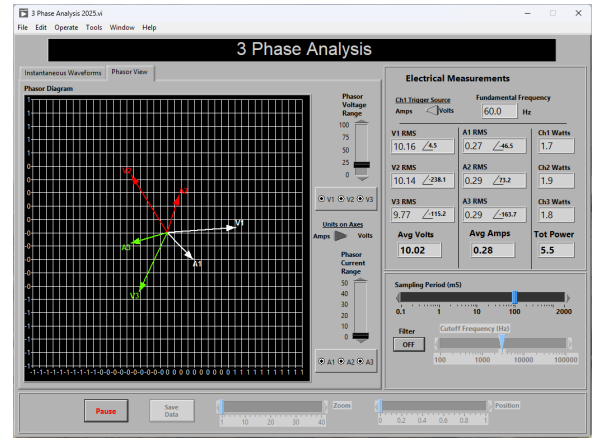
(a) Waveform of circuit with RL balanced load, neutrals disconnected.



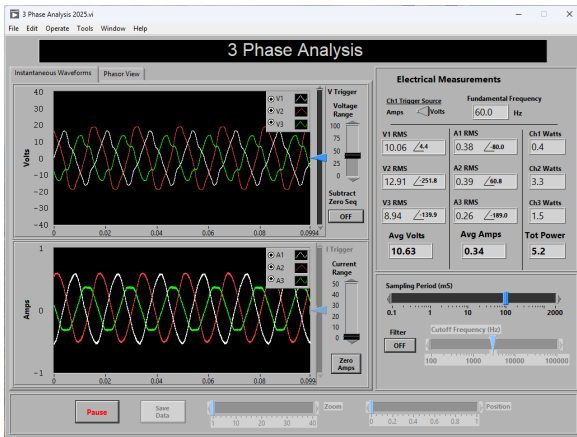(b) Phasor view of circuit with RL balanced load, neutrals disconnected.




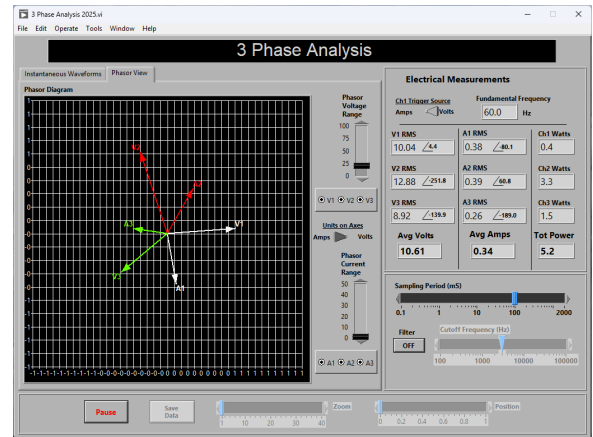(c) Waveform of circuit with RL unbalanced load, shorted resistor, neutrals disconnected.




(d) Phasor view of circuit with RL unbalanced load, shorted resistor, neutrals disconnected.


Figure 6. Three-phase measurements with wye-connected RL load box (Task 2A).

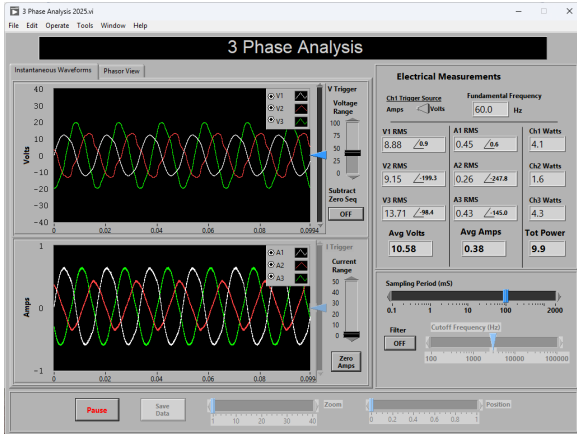

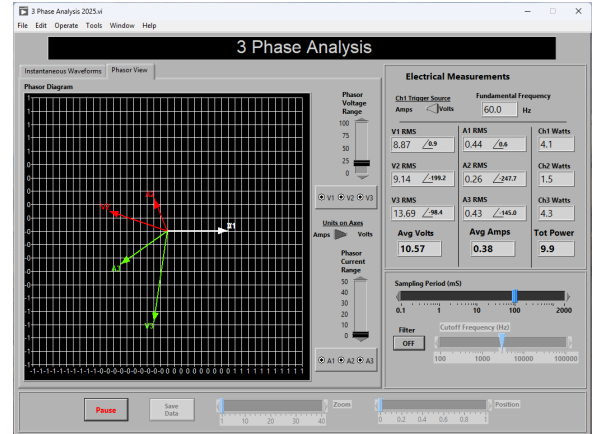
(e) Waveform of circuit with RL unbalanced load, shorted inductor, neutrals disconnected.



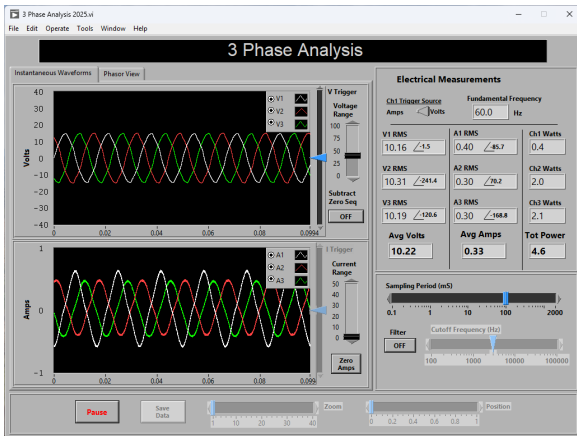
(f) Phasor view of circuit with RL unbalanced load, shorted inductor, neutrals disconnected.



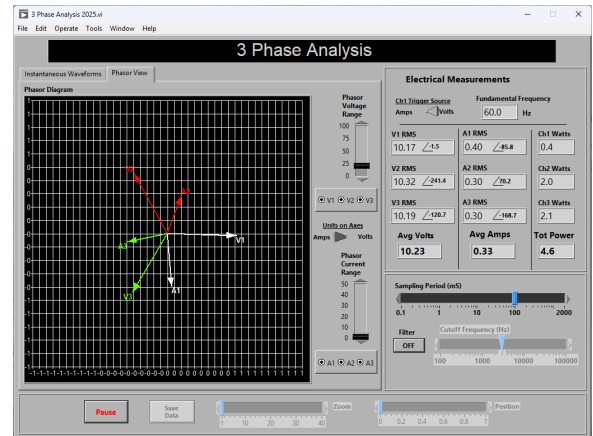
(g) Waveform of circuit with RL unbalanced load, shorted resistor, neutrals connected.



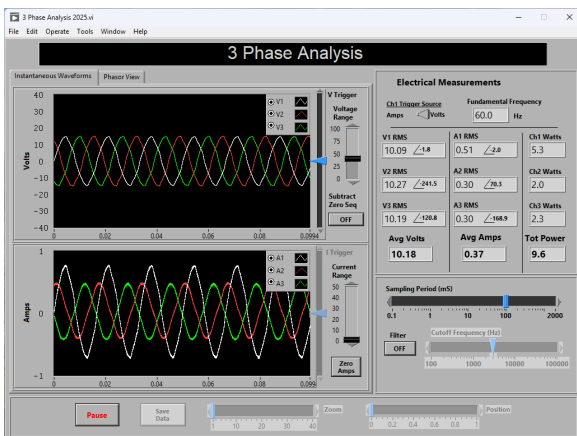(h) Phasor view of circuit with RL unbalanced load, shorted resistor, neutrals connected.




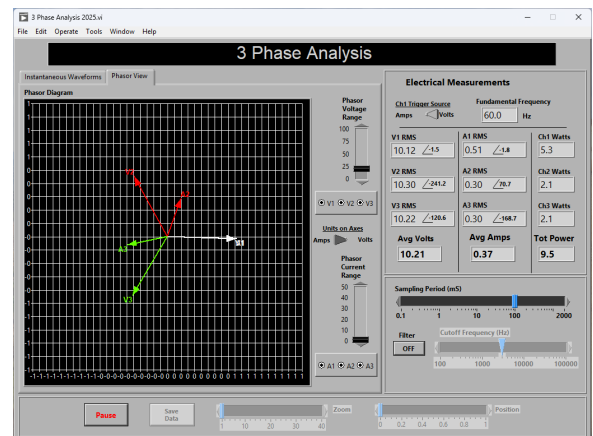(i) Waveform of circuit with RL unbalanced load, shorted inductor, neutrals connected.




(j) Phasor view of circuit with RL unbalanced load, shorted inductor, neutrals connected.


Figure 6. Three-phase measurements with wye-connected RL load box (Task 2A).

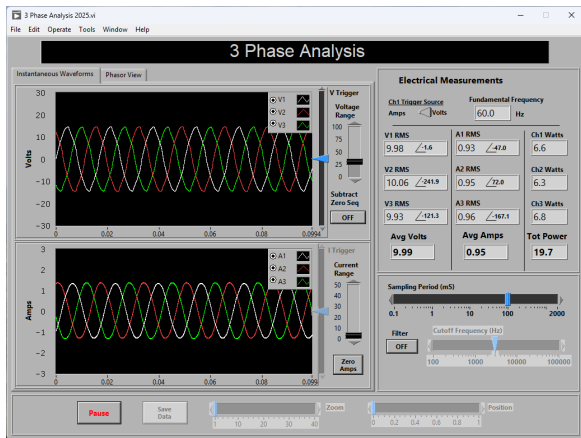

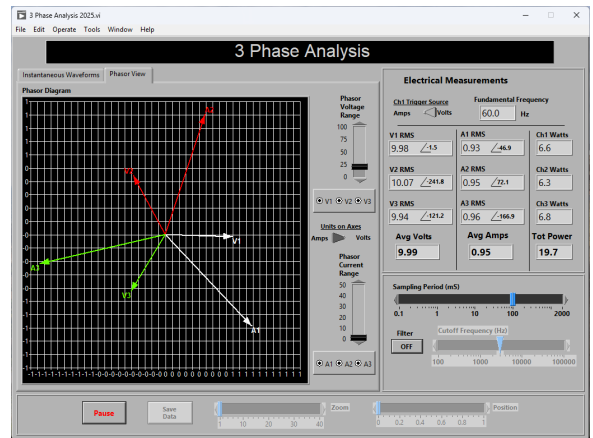
(a) Waveform of circuit with RL balanced load.



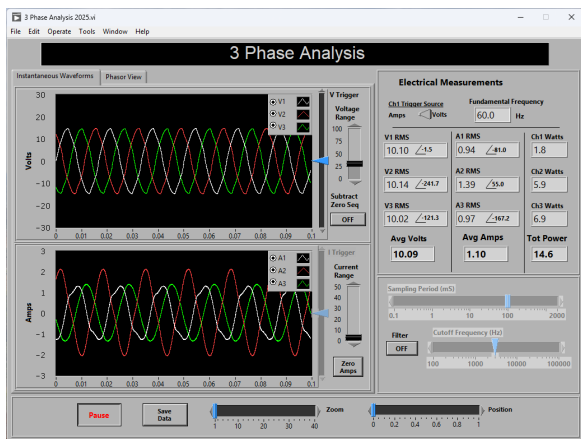
(b) Phasor view of circuit with RL balanced load.



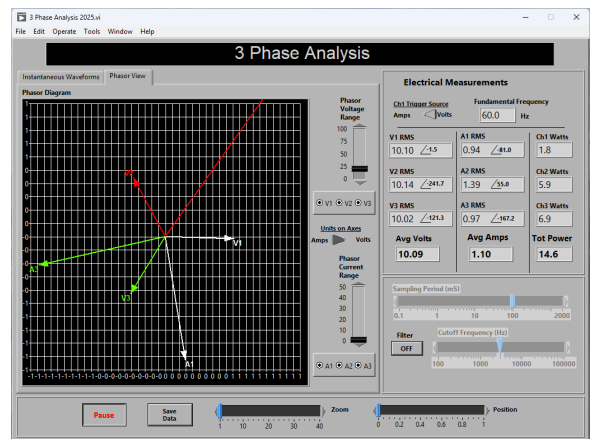
(c) Waveform of circuit with RL unbalanced load, shorted resistor.



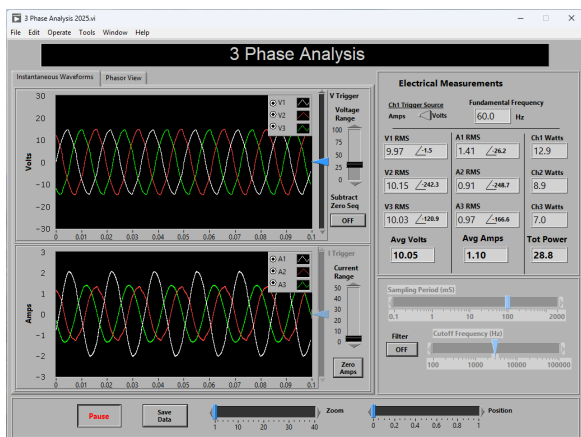(d) Phasor view of circuit with RL unbalanced load, shorted resistor.




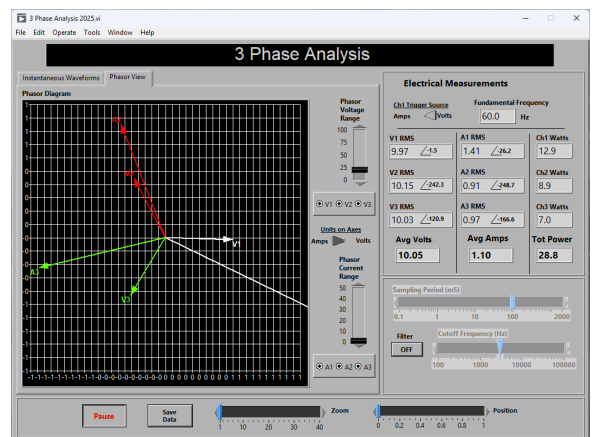(e) Waveform of circuit with RL unbalanced load, shorted inductor.




(f) Phasor view of circuit with RL unbalanced load, shorted inductor.


Figure 7. Three-phase measurements with delta-connected RL load box (Task 2B).

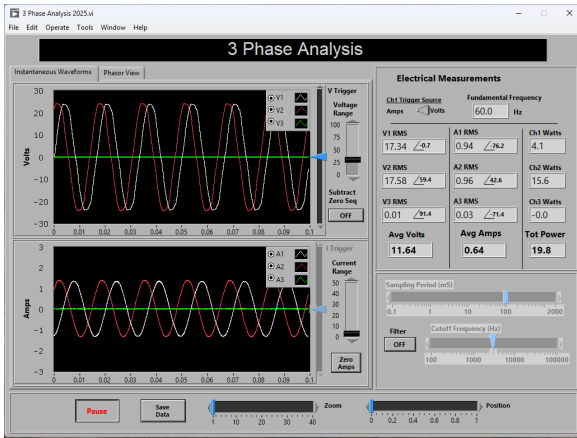

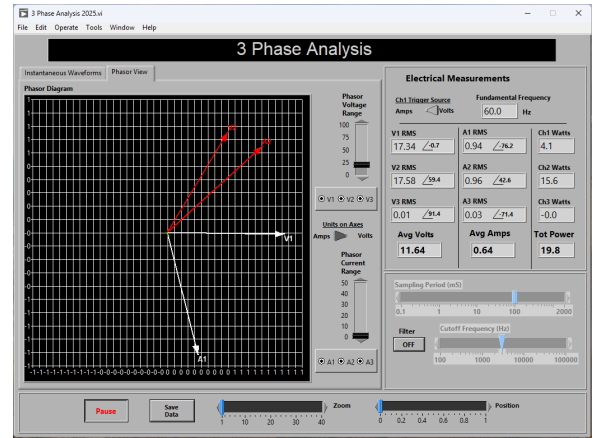
(a) Waveform of circuit with RL balanced load.



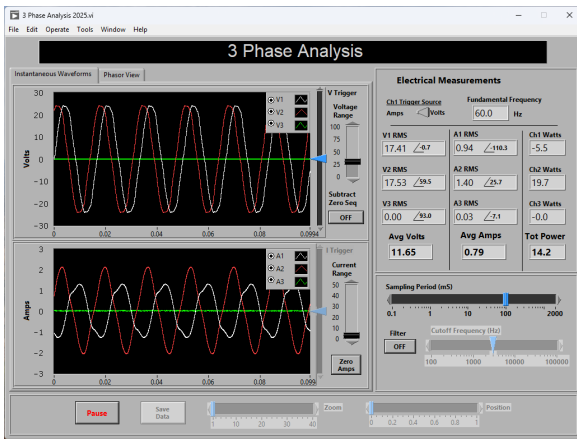
(b) Phasor view of circuit with RL balanced load.



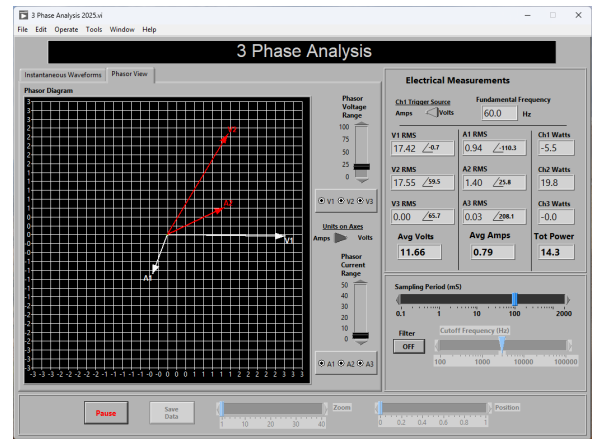
(c) Waveform of circuit with RL unbalanced load, shorted resistor.



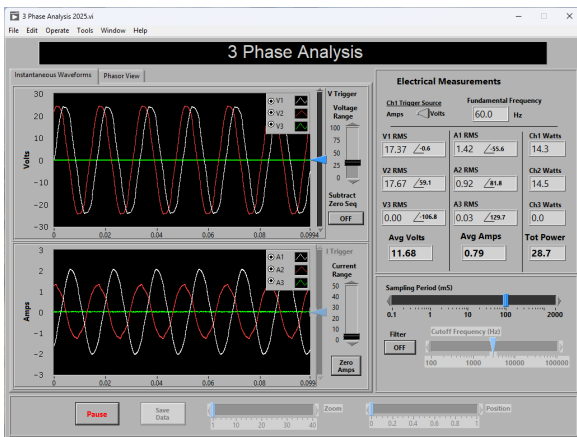(d) Phasor view of circuit with RL unbalanced load, shorted resistor.




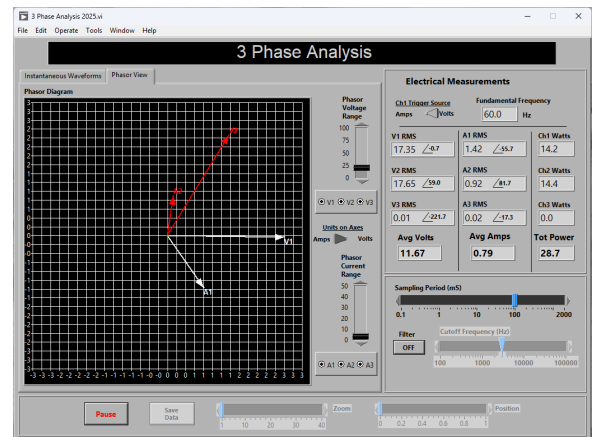(e) Waveform of circuit with RL unbalanced load, shorted inductor.




(f) Phasor view of circuit with RL unbalanced load, shorted inductor.


Figure 8. Two-wattmeter measurements with delta-connected RL load box (Task 2C).

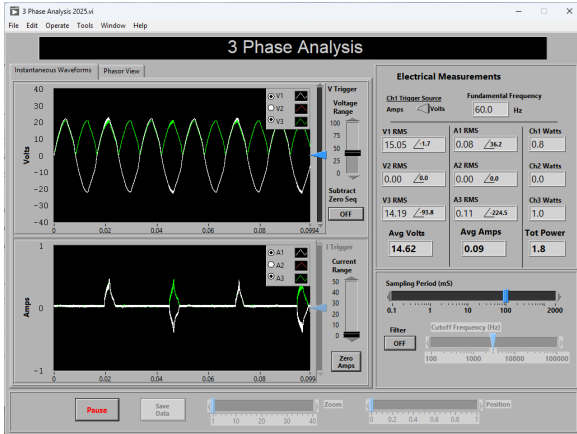

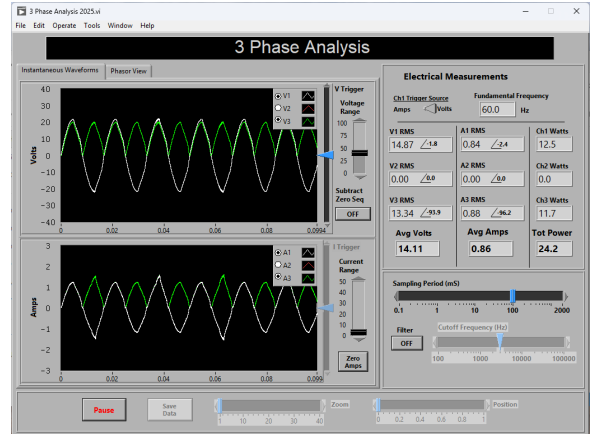
(a) Waveform of circuit without a capacitor filter under no load.



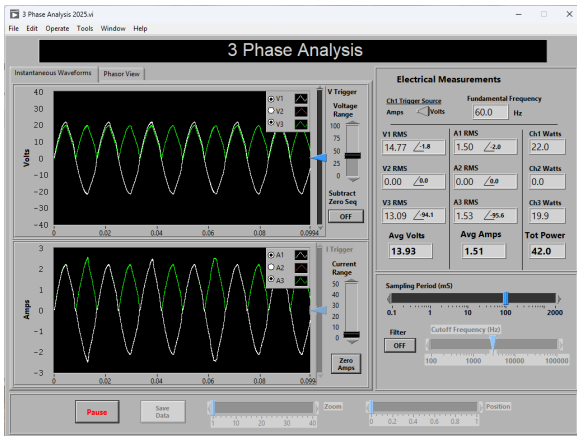
(b) Waveform of circuit without a capacitor filter under half load.



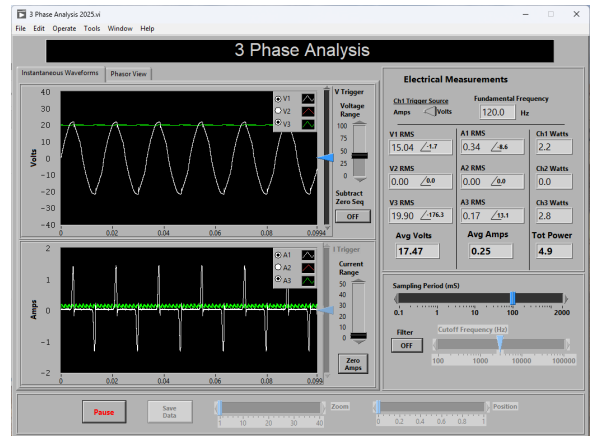
(c) Waveform of circuit without a capacitor filter under full load.



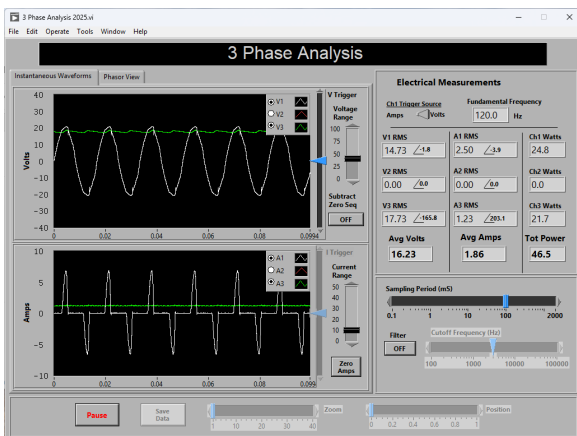(d) Waveform of circuit with a capacitor filter under no load.




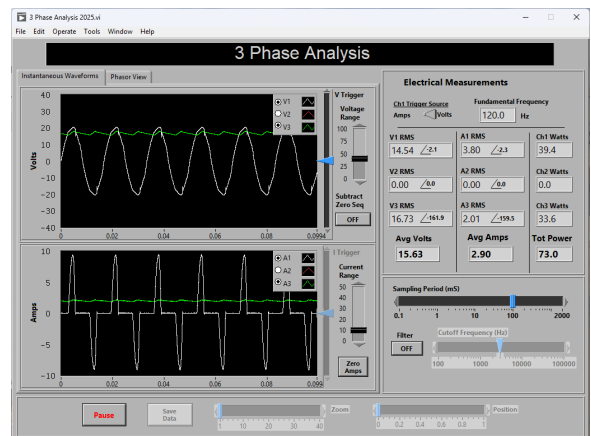(e) Waveform of circuit with a capacitor filter under half load.




(f) Waveform of circuit with a capacitor filter under full load.


Figure 9. Single-phase full-wave rectifier, without and with capacitor filter (Task 3A).

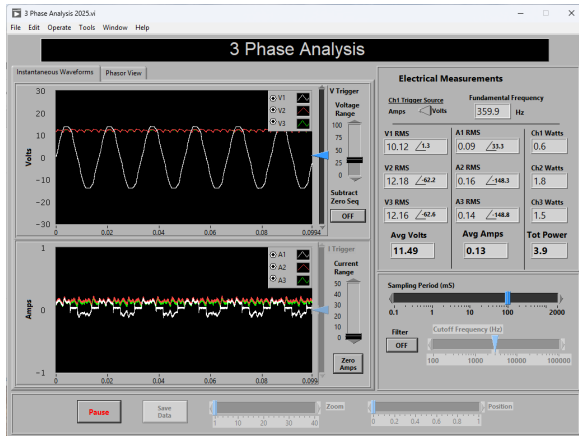

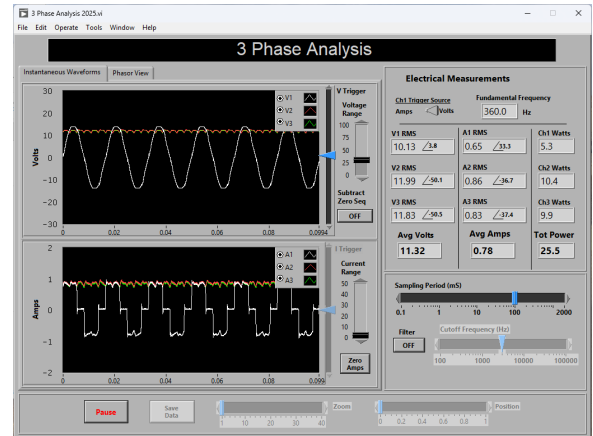
(a) Waveform of circuit without a capacitor filter under no load.



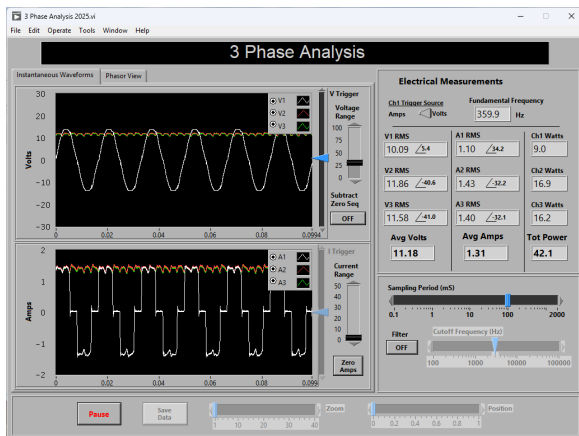
(b) Waveform of circuit without a capacitor filter under half load.



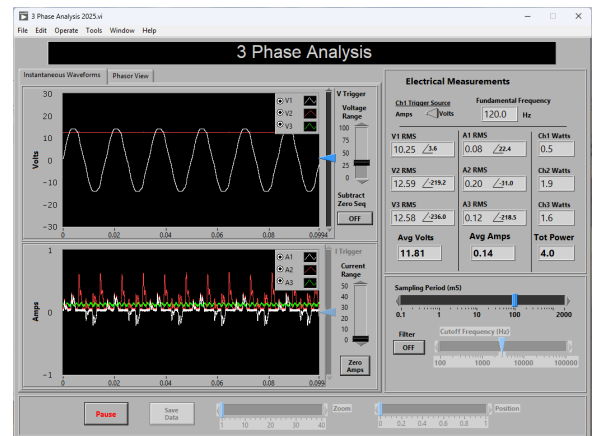
(c) Waveform of circuit without a capacitor filter under full load.



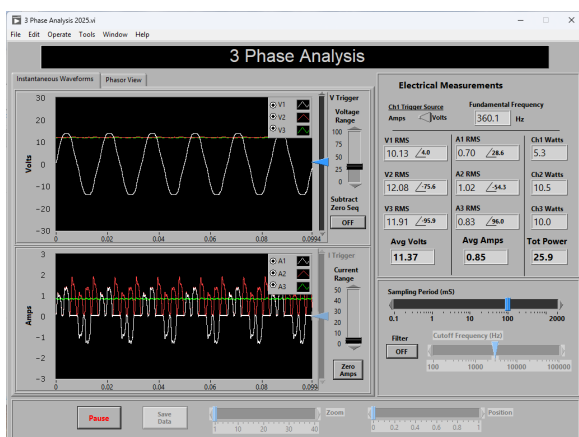(d) Waveform of circuit with a capacitor filter under no load.



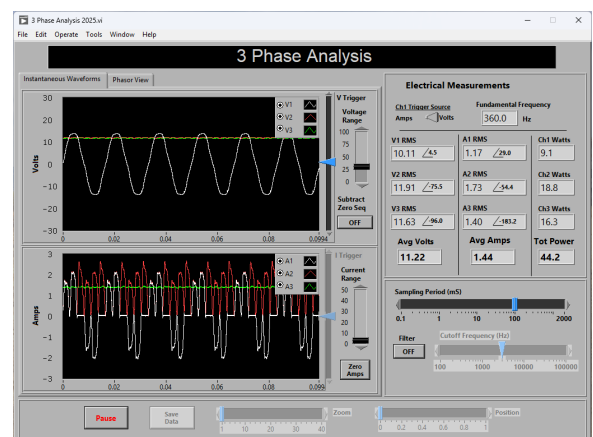(e) Waveform of circuit with a capacitor filter under half load.



(f) Waveform of circuit with a capacitor filter under full load.

Figure 10. Three-phase full-wave rectifier, without and with capacitor filter (Task 4A).